

# **Excellent Integrated System Limited**

Stocking Distributor

Click to view price, real time Inventory, Delivery & Lifecycle Information:

Texas Instruments TPA6120A2DWP

For any questions, you can email us directly: <u>sales@integrated-circuit.com</u>

## Distributor of Texas Instruments: Excellent Integrated System Limited

Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com



Sample & Buy

Product

Folder

Technical Documents

🖉 Tools & Software

**TPA6120A2** 

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015

# **TPA6120A2 High Fidelity Headphone Amplifier**

#### 1 Features

**Texas** 

SNR of 128dB A-Weighted.

**INSTRUMENTS** 

- THD of 112.5dB
- Current-Feedback Architecture
- Output Voltage Noise of 0.9µVrms at Gain = 1V/V (16 $\Omega$  Load)
- Power Supply Range: ±5V to ±15V
- 1300V/µs Slew Rate
- Can be configured for Single Ended or Differential Inputs
- Independent Power Supplies for Low Crosstalk

#### Applications 2

- Professional Audio Equipment
- HiFi Smartphone
- **Consumer Home Audio Equipment**
- **Headphone Drivers**

## 3 Description

In applications requiring a high-power output, very high fidelity headphone amplifier, the TPA6120A2 replaces a costly discrete design and allows music, not the amplifier, to be heard. The TPA6120A2's current-feedback AB amplifier architecture delivers high bandwidth, extremely low noise, and up to 128dB of dynamic range.

Support &

Community


Three key features make current-feedback amplifiers outstanding for audio. The first feature is the high rate that prevents odd order distortion slew anomalies. The second feature is current-on-demand at the output that enables the amplifier to respond quickly and linearly when necessary without risk of output distortion. When large amounts of output power are suddenly needed, the amplifier can respond extremely quickly without raising the noise floor of the system and degrading the signal-to-noise ratio. The third feature is the gain-independent frequency response that allows the full bandwidth of the amplifier to be used over a wide range of gain settings.

#### Device Information<sup>(1)</sup>

PART NUMBER	PACKAGE	BODY SIZE (NOM)
TPA6120A2	HSOP (20)	7.5mm x 12.82mm
	VQFN (14)	3.5mm x 3.5mm

(1) For all available packages, see the orderable addendum at the end of the datasheet.

#### Simplified Schematic 4

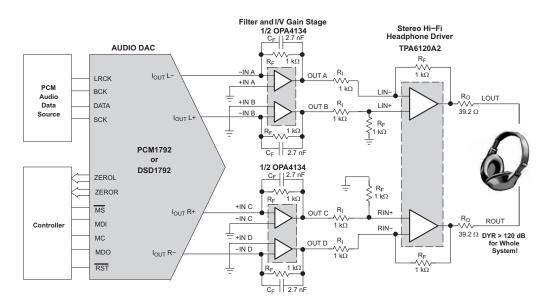



**Table of Contents** 

#### TPA6120A2

SLOS431B-MARCH 2004-REVISED FEBRUARY 2015



www.ti.com

Page

1 2 3 4	App Des Sim	tures
5		ision History
6		Configuration and Functions 3
7	Spe	cifications4
	7.1	Absolute Maximum Ratings 4
	7.2	ESD Ratings 4
	7.3	Recommended Operating Conditions 4
	7.4	Thermal Information 4
	7.5	Electrical Characteristics5
	7.6	Operating Characteristics5
	7.7	Typical Characteristics6
8	Para	ameter Measurement Information
9	Deta	ailed Description
	9.1	Overview
	9.2	Functional Block Diagram 8

	9.3	Feature Description	8
	9.4	Device Functional Modes	9
10	Арр	lications and Implementation	9
	10.1	Application Information	9
	10.2	Typical Application	9
11	Pow	er Supply Recommendations	16
	11.1	Independent Power Supplies	16
	11.2	Power Supply Decoupling	16
12	Layo	out	17
	12.1	Layout Guidelines	17
	12.2	Layout Example	18
13	Devi	ice and Documentation Support	20
	13.1	Documentation Support	20
	13.2	Trademarks	20
	13.3	Electrostatic Discharge Caution	20
	13.4	Glossary	20
14	Мес	hanical, Packaging, and Orderable	
	Infor	mation	20

### 5 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

C	hanges from Revision A (July 2014) to Revision B F	Page
•	Changed the Device Information Packages From: DWP (20) and RGY (14) To: HSOP (20) and VQFN (14)	1
•	Changed QFN to VQFN in the Pin Functions table	3
•	Added a NOTE to the Applications and Implementation section	9
•	Added Title: Application Information	9
•	Deleted Title: Application Circuit	9
•	Changed the Design Requirements	10
•	Deleted Title: Application Circuit	14
•	Moved two paragraphs following Figure 19 to proceed Figure 19	14

#### Changes from Original (March 2004) to Revision A

•	Changed Added ESD Rating table, Feature Description section, Device Functional Modes, Application and Implementation section, Power Supply Recommendations section, Layout section, Device and Documentation	
	Support section, and Mechanical, Packaging, and Orderable Information section	1
•	Added the VQFN package information	1
•	Updated Pin descriptions to clarify power supply.	3
•	Lowered minimum V <sub>IC</sub> (±5Vcc) From: ±3.6 To: ±3.4	5
•	Lowered minimum V <sub>IC</sub> (±15Vcc) From: ±13.4V To: ±13.2V	5
•	Deleted IMD (Intermodulation Distortion), ±12Vcc data, Dynamic Range (replaced with SNR, in 1V/V gain)	5
•	Changed the THD=N UNIT From: % To: dB	. 5
•	Changed the SNR to show the latest data from newer QFN based EVM	5




**Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com


www.ti.com

#### TPA6120A2

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015

# 6 Pin Configuration and Functions

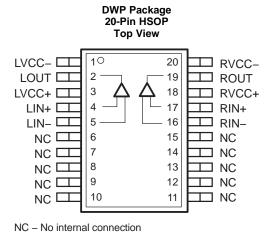

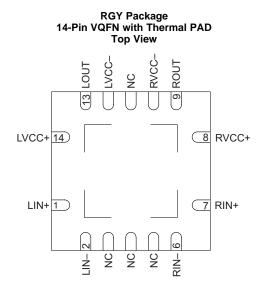

#### **Pin Functions**

PIN			1/0	DECODIDITIONO	
NAME	HSOP NO.	VQFN NO.	I/O	DESCRIPTIONS	
LVCC-	1	12	I	Left channel negative power supply – must be kept at the same potential as RVCC- if both amplifiers are to be used.	
LOUT	2	13	0	Left channel output	
LVCC+	3	14	I	Left channel positive power supply – must be kept at the same potential as RVCC+ if both amplifiers are to be used.	
LIN+	4	1	I	Left channel positive input	
LIN-	5	2	I	Left channel negative input	
NC	6,7,8,9,10,11, 12,13,14,15	3, 4, 5, 11	-	Not internally connected	
RIN-	16	6	I	Right channel negative input	
RIN+	17	7	I	Right channel positive input	
RVCC+	18	8	I	Right channel positive power supply - must be kept at the same potential as LVCC+ if both amplifiers are to be used.	
ROUT	19	9	0	Right channel output	
RVCC-	20	10	I	Right channel negative power supply - must be kept at the same potential as LVCC- if both amplifiers are to be used.	
Thermal Pad	-	-	-	Connect to ground. The thermal pad must be soldered down in all applications to properly secure device on the PCB.	

3



TEXAS INSTRUMENTS

#### TPA6120A2

SLOS431B-MARCH 2004-REVISED FEBRUARY 2015

www.ti.com

#### 7 Specifications

### 7.1 Absolute Maximum Ratings

over operating free-air temperature range (unless otherwise noted) <sup>(1)</sup>

	MIN	MAX	UNIT
Supply voltage, $xV_{CC+}$ to $xV_{CC-}$ Where x=L or R channel	9	33	V
Input voltage, VI <sup>(2)</sup>		$\pm V_{CC}$	
Differential input voltage, VID		6	V
Minimum load impedance		8	Ω
Continuous total power dissipation	See Therma	See Thermal Information	
Operating free-air temperature range, T <sub>A</sub>	-40	85	°C
Operating junction temperature range, T <sub>J</sub> <sup>(3)</sup>	-40	150	°C
Storage Temperature, T <sub>stg</sub>	-40	125	°C

(1) Stresses beyond those listed under "absolute maximum ratings" may cause permanent damage to the device. These are stress ratings only, and functional operation of the device at these or any other conditions beyond those indicated under "recommended operating conditions" is not implied. Exposure to absolute-maximum-rated conditions for extended periods may affect device reliability.

(2) When the TPA6120A2 is powered down, the input source voltage must be kept below 600mV peak.

(3) The TPA6120A2 incorporates an exposed PowerPAD on the underside of the chip. This acts as a heatsink and must be connected to a thermally dissipating plane for proper power dissipation. Failure to do so may result in exceeding the maximum junction temperature that could permanently damage the device. See TI Technical Brief SLMA002 for more information about utilizing the PowerPAD thermally enhanced package.

#### 7.2 ESD Ratings

				VALUE	UNIT
V(FOR)		Human body model (HBM), per ANSI/ESDA/JEDEC JS-001 <sup>(1)</sup>	For Pins: LVCC+, RVCC+, LVCC-, RVCC	±500	
	Electrostatic Discharge		For all pins except: LVCC+, RVCC+, LVCC-, RVCC	±2000	V
		Charged device model (CDM), per JEDEC specification J	ESD22-C101	±1500	

(1) Level listed above is the passing level per ANSI, ESDA, and JEDEC JS-001. JEDEC document JEP155 states that 500V HBM allows safe manufacturing with a standard ESD control process.

### 7.3 Recommended Operating Conditions

		MIN	NOM MAX	UNIT
	Split Supply	±5	±15	V
Supply voltage, $V_{CC+}$ and $V_{CC-}$	Single Supply	10	30	V
Load impedance	$V_{CC} = \pm 5V \text{ or } \pm 15V$	16		Ω
Operating free-air temperature, T <sub>A</sub>		-40	85	°C

#### 7.4 Thermal Information

		TPA6120A2	TPA6120A2	
	THERMAL METRIC <sup>(1)</sup>	DWP [HSOP]	RGY [VQFN]	UNIT
		20 PINS	14 PINS	
$R_{\thetaJA}$	Junction-to-ambient thermal resistance	44.5	49.4	
R <sub>0JCtop</sub>	Junction-to-case (top) thermal resistance	55.2	62.0	
R <sub>θJB</sub>	Junction-to-board thermal resistance	36.1	25.4	00 AM
Ψ <sub>JT</sub>	Junction-to-top characterization parameter	23.1	1.6	°C/W
Ψ <sub>JB</sub>	Junction-to-board characterization parameter	36.2	25.5	
R <sub>0JCbot</sub>	Junction-to-case (bottom) thermal resistance	7.6	6.2	

(1) For more information about traditional and new thermal metrics, see the IC Package Thermal Metrics application report, SPRA953.



www.ti.com

#### **TPA6120A2**

SLOS431B-MARCH 2004-REVISED FEBRUARY 2015

#### 7.5 Electrical Characteristics

over operating free-air temperature range (unless otherwise noted)

	PARAMETER	TEST CONDITIONS	MIN	ТҮР	MAX	UNIT
V <sub>IO</sub>	Input offset voltage (measured differentially)	$V_{CC} = \pm 5V \text{ or } \pm 15V$		2	5	mV
PSRR	Power supply rejection ratio	$V_{CC} = \pm 5V \text{ to} \pm 15V$		75		dB
V	Common mode input veltere	$V_{CC} = \pm 5V$	±3.4	±3.7		V
V <sub>IC</sub>	Common mode input voltage	$V_{CC} = \pm 15V$	±13.2	±13.5		v
		$V_{CC} = \pm 5V$		11.5	13	mA
ICC	Supply current (each channel)	$V_{CC}=\pm 15V$			15	
I <sub>O</sub>	Output current (per channel)	$V_{CC}$ = ±5V to ±15V		700		mA
	Input offset voltage drift	$V_{CC} = \pm 5V \text{ or } \pm 15V$		20		µV/°C
r <sub>i</sub>	Input resistance			300		kΩ
r <sub>o</sub>	Output resistance	Open Loop		13		Ω
Vo	Output voltage swing	$V_{CC} = \pm 15V, R_L = 25\Omega$	11.8 to -11.5	12.5 to -12.2		V

### 7.6 Operating Characteristics<sup>(1)</sup>

 $T_A = 25^{\circ}C$ ,  $R_L = 25\Omega$ , Gain = 1V/V (unless otherwise noted)

	PARAMETER	TEST	CONDITIONS	MIN	TYP	MAX	UNIT	
		$R_1 = 32\Omega$	$V_{CC} = \pm 5V P_O = 10mW$		101			
		f = 1kHz	$V_{CC} = \pm 15V P_{O} = 100mW$		90		-	
		$R_1 = 64\Omega$	$V_{CC} = \pm 5V P_O = 10mW$		104			
		f = 1kHz	$V_{CC} = \pm 15 V P_{O} = 100 mW$		94			
THD+N	Total harmonic distortion plus noise	V <sub>CC</sub> = ±5V, Gain = 1V/V	$V_{O} = 3V_{PP},$ $R_{L} = 10k\Omega$ f = 1kHz		104		dB	
		$V_{CC} = \pm 15V,$ Gain = 1V/V	$V_{O} = 10V_{PP},$ $R_{L} = 10k\Omega$ f = 1kHz		108			
		$V_{CC} = \pm 15V,$ Gain = 1V/V	$V_{O} = 2V_{PP},$ $R_{L} = 10k\Omega$ f = 1kHz		112.5			
	Supply voltage rejection ratio	$R_L = 32\Omega$	$V_{CC} = \pm 5V$		-75		dB	
		f = 1kHz V <sub>(RIPPLE)</sub> = 1V <sub>PP</sub>	$V_{CC}=\pm 15V$		-78			
k <sub>SVR</sub>		ratio $R_L = 64\Omega$	V <sub>CC</sub> = ±5V		-75			
		f = 1kHz V <sub>(RIPPLE)</sub> = 1V <sub>PP</sub>	$V_{CC}=\pm 15V$		-75			
CMRR	Common mode rejection ratio (differential)	$V_{CC} = \pm 5V \text{ or } \pm 15V$			100		dB	
00		$V_{CC} = \pm 15V$ , Gain = 5V/V	/, V <sub>O</sub> = 20 V <sub>PP</sub>		1300		Mue	
SR	Slew rate	$V_{CC} = \pm 5V$ , Gain = 2V/V,	$V_{O} = 5 V_{PP}$		900		V/µs	
Vn	Output noise voltage	$V_{CC} = \pm 5V$ to $\pm 15V$ $R_L = 16\Omega$	Gain = 1V/V		0.9		µVrms	
		$R_1 = 32\Omega$ to $64\Omega$	V <sub>CC</sub> = ±15V, Gain = 1V/V. A Weighted		128		٦Ŀ	
SNR	Signal-to-noise ratio	f = 1kHz	$V_{CC} = \pm 5V$ , Gain = 1V/V. A Weighted		116		dB	
		$V_{I} = 1V_{RMS}$	$V_{CC} = \pm 15V$		-112			
	Crosstalk	$R_F = 1kΩ$ $R_L = 32Ω$ to $64Ω$ f = 1kHz	$V_{CC} = \pm 5V$		-105		dB	

(1) For THD+N, k<sub>SVR</sub>, and crosstalk, the bandwidth of the measurement instruments was set to 80kHz.



#### **Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com


TEXAS INSTRUMENTS

www.ti.com

TPA6120A2

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015

## 7.7 Typical Characteristics

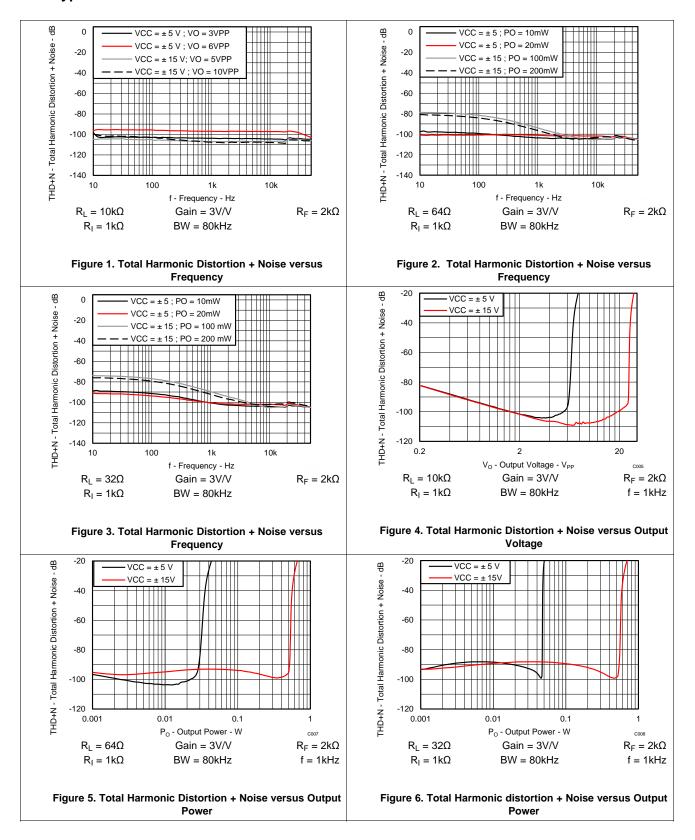

Copyright  $\ensuremath{\mathbb{C}}$  2004–2015, Texas Instruments Incorporated




**Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com

www.ti.com

TPA6120A2

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015

#### Typical Characteristics (continued)

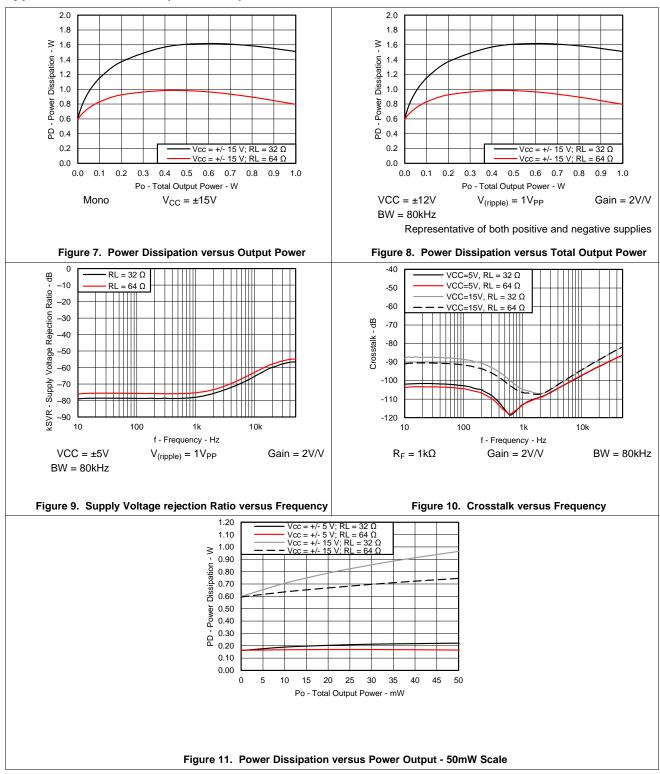

7






SLOS431B – MARCH 2004 – REVISED FEBRUARY 2015



www.ti.com

#### 8 Parameter Measurement Information

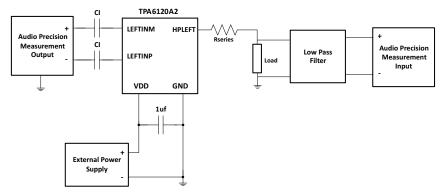

- A. Separate power supply decoupling capacitors are used on all Vcc pins.
- B. The low-pass filter is used to remove harmonic content above the audible range.


#### Figure 12. Test Circuit

### 9 Detailed Description

#### 9.1 Overview

The TPA6120A2 is a current-feedback amplifier with differential inputs and single-ended outputs.

#### 9.2 Functional Block Diagram

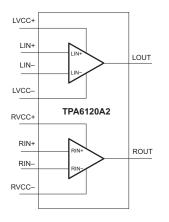

#### 9.3 Feature Description

#### 9.3.1 Current-Feedback Amplifier

Current feedback results in low voltage noise, low distortion, high open-loop gain throughout a large frequency range, and can be used in a similar fashion as voltage-feedback amplifiers. The low distortion of the TPA6120A2 results in a signal-to-noise ratio of 128 dB.

#### 9.3.2 Independent Power Supplies

Because the power supplies for the two amplifiers are available separately, one amplifier can be turned off to conserve power.

See Power Supply Recommendations.

Submit Documentation Feedback

8



**Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com

www.ti.com

**TPA6120A2** SLOS431B – MARCH 2004 – REVISED FEBRUARY 2015

#### 9.4 Device Functional Modes

INSTRUMENTS

This device operates as a wide-bandwidth, current-feedback amplifier.

#### **10** Applications and Implementation

#### NOTE

Information in the following applications sections is not part of the TI component specification, and TI does not warrant its accuracy or completeness. TI's customers are responsible for determining suitability of components for their purposes. Customers should validate and test their design implementation to confirm system functionality.

#### **10.1** Application Information

In many applications, the audio source is digital, and must go through a digital-to-analog converter (DAC) so that traditional analog amplifiers can drive the speakers or headphones.

#### **10.2 Typical Application**

#### 10.2.1 High Voltage, High Fidelity DAC + Headphone Amplifier Solution

Figure 13 shows a complete circuit schematic for such a system. The digital audio is fed into a high performance DAC. The PCM1792, a Burr-Brown product from TI, is a 24-bit, stereo DAC.

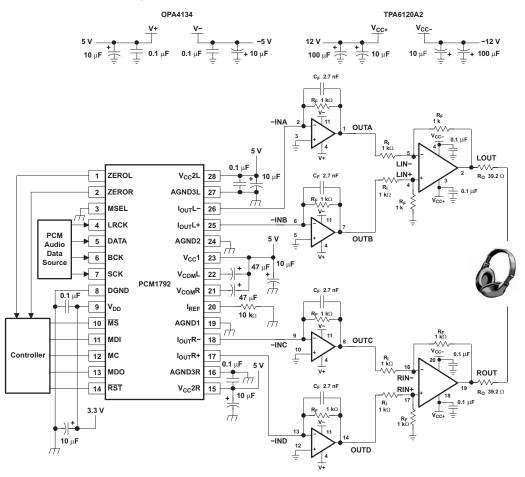


Figure 13. Typical Application Circuit

Copyright © 2004–2015, Texas Instruments Incorporated



#### TPA6120A2

SLOS431B-MARCH 2004-REVISED FEBRUARY 2015



www.ti.com

#### **Typical Application (continued)**

- 10.2.1.1 Design Requirements
- ±12V Operation from bipolar power supply
- Differential voltage source
- Be transparent to the user

#### 10.2.1.2 Detailed Design Procedure

The output of the PCM1792 is current, not voltage, so the OPA4134 is used to convert the current input to a voltage output. The OPA4134 (SBOS058), is a low-noise, high-speed, high-performance operational amplifier.  $C_F$  and  $R_F$  are used to set the cutoff frequency of the filter. The RC combination in Figure 13 has a cutoff frequency of 59 kHz. All four amplifiers of the OPA4134 are used so the TPA6120A2 can be driven differentially.

The output of the OPA4134 goes into the TPA6120A2. The TPA6120A2 is configured for use with differential inputs, stereo use, and a gain of 2V/V. Note that the  $0.1\mu$ F capacitors are placed at every supply pin of the TPA6120A2, as well as the  $39.2\Omega$  series output resistor.

Each output goes to one channel of a pair of stereo headphones, where the listener enjoys crisp, clean, virtually noise free music with a dynamic range greater than the human ear is capable of detecting.

#### 10.2.1.2.1 Resistor Values

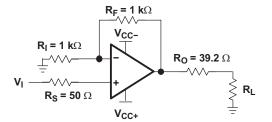


Figure 14. Single-Ended Input With A Noninverting Gain Of 2V/V

In the most basic configuration (see Figure 14), four resistors must be considered, not including the load impedance. The feedback and input resistors,  $R_F$  and  $R_I$ , respectively, determine the closed-loop gain of the amplifier.  $R_O$  is a series output resistor designed to protect the amplifier from any capacitance on the output path, including board and load capacitance.  $R_S$  is a series input resistor.

The series output resistor should be between  $10\Omega$  and  $100\Omega$ . The output series resistance eases the work of the output power stage by increasing the load when low impedance headphones are connected, as well as isolating any capacitance on the following traces and headphone cable.

Because the TPA6120A2 is a current-feedback amplifier, take care when choosing the feedback resistor. TI recommends a lower level of  $800\Omega$  for the feedback resistance. No capacitors should be used in the feedback path, as they will form a short circuit at high frequencies.

The value of the feedback resistor should be chosen by using Figure 17 as a guideline. The gain can then be set by adjusting the input resistor. The smaller the feedback resistor, the less noise is introduced into the system. However, smaller values move the dominant pole to higher and higher frequencies, making the device more susceptible to oscillations. Higher feedback resistor values add more noise to the system, but pull the dominant pole down to lower frequencies, making the device more stable. Higher impedance loads tend to make the device more unstable. One way to combat this problem is to increase the value of the feedback resistor. It is not recommended that the feedback resistor exceed a value of  $10k\Omega$ . The typical value for the feedback resistor for the TPA6120A2 is  $1k\Omega$ . In some cases, where a high-impedance load is used along with a relatively large gain and a capacitive load, it may be necessary to increase the value of the feedback resistor from  $1k\Omega$  to  $2k\Omega$ , thus adding more stability to the system. Another method to deal with oscillations is to increase the size of  $R_0$ .

#### CAUTION

Do not place a capacitor in the feedback path. Doing so can cause oscillations.



#### www.ti.com

**TPA6120A2** 

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015

#### Typical Application (continued)

Capacitance at the outputs can cause oscillations. Capacitance from some sources, such as layout, can be minimized. Other sources, such as those from the load (for example, the inherent capacitance in a pair of headphones), cannot be easily minimized. In this case, adjustments to  $R_{O}$  and/or  $R_{F}$  may be necessary.

The series output resistor should be kept at a minimum of  $10\Omega$ ; small enough so that the effect on the load is minimal, but large enough to provide the protection necessary such that the output of the amplifier sees little capacitance. The value can be increased to provide further isolation, up to  $100\Omega$ . Care should be taken in selecting the thermal capacity of the output series resistor, as it will create a potential divider with the load and dissipate power.

The series resistor, R<sub>S</sub>, should be used for two reasons:

- 1. It prevents the positive input pin from being exposed to capacitance from the line and source.
- 2. It prevents the source from seeing the input capacitance of the TPA6120A2.

The 50 $\Omega$  resistor was chosen because it provides ample protection without interfering in any noticeable way with the signal. Not shown is another 50 $\Omega$  resistor that can be placed on the source side of R<sub>S</sub> to ground. In that capacity, it serves as an impedance match to any 50 $\Omega$  source. See Figure 15.


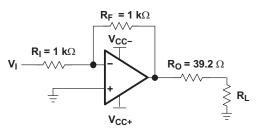


Figure 15. Single-Ended Input With A Noninverting Gain Of –1V/V

Figure 16 shows the TPA6120A2 connected with differential inputs. Differential inputs are useful because they take the greatest advantage of the high CMRR of the device. The two feedback resistor values must be kept the same, as do the input resistor values.

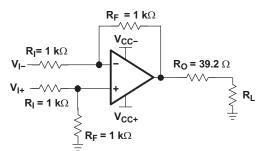



Special note regarding mono operation:

- If both amplifiers are powered on, but only one channel is to be used, the unused amplifier MUST have a feedback resistor from the output to the negative input. Additionally, the positive input should be grounded as close to the pin as possible. Terminate the output as close to the output pin as possible with a 25Ω load to ground.
- These measures should be followed to prevent the unused amplifier from oscillating. If it oscillates, and the power pins of both amplifiers are tied together, the performance of the amplifier could be seriously degraded.



#### TPA6120A2

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015



www.ti.com


#### **Typical Application (continued)**

#### 10.2.1.2.2 Checking For Oscillations And Instability

Checking the stability of the amplifier setup is recommended. High frequency oscillations in the megahertz region can cause undesirable effects in the audio band.

Sometimes, the oscillations can be quite clear. An unexpectedly large draw from the power supply may be an indication of oscillations. These oscillations can be seen with an oscilloscope. However, if the oscillations are not obvious, or there is a chance that the system is stable but close to the edge, placing a scope probe with 10pF of capacitance can make the oscillations worse, or actually cause them to start.

A network analyzer can be used to determine the inherent stability of a system. An output versus frequency curve generated by a network analyzer can be a good indicator of stability. At high frequencies, the curve shows whether a system is oscillating, close to oscillation, or stable. In Figure 17 the system is stable because the high frequency rolloff is smooth and has no peaking. Increasing  $R_F$  decreases the frequency at which this rolloff occurs (see the Resistor Values section). Another scenario shows some peaking at high frequency. If the peaking is 2dB, the amplifier is stable as there is still 45 degrees of phase margin. As the peaking increases, the phase margin shrinks, causing the amplifier and the system to approach instability. The same system that normally has a 2dB peak has an increased peak when a capacitor is added to the output, indicating that the system is either on the verge of oscillation or is oscillating; corrective action is required.

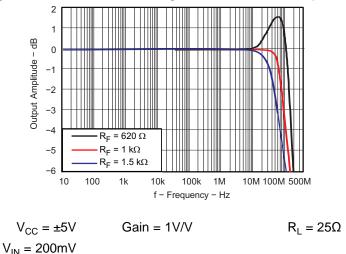





Contact us: sales@integrate

www.ti.com

TPA6120A2

(2)

SLOS431B-MARCH 2004-REVISED FEBRUARY 2015

### **Typical Application (continued)**

#### 10.2.1.2.3 Thermal Considerations

**INSTRUMENTS** 

There is no one to one relationship between output power and heat dissipation, so the following equations must be used:

Efficiency of an amplifier =  $\frac{P_L}{P_{SUP}}$  (1)

#### Where

$$P_L = \frac{V_{LRMS}^2}{R_L}$$
, and  $V_{LRMS} = \frac{V_P}{\sqrt{2}}$ , therefore,  $P_L = \frac{V_P^2}{2R_L}$  per channel

$$PSUP = VCC \ CCavg + VCC \ CC(q)$$
(3)  
$$HCCavg = \frac{1}{2} \int_{-\infty}^{\frac{\pi}{2}} \frac{V_P}{V_P} \sin(t) \, dt = -\frac{V_P}{V_P} [\cos(t)]^{\frac{\pi}{2}} = \frac{V_P}{V_P}$$

$$I_{CCavg} = \frac{1}{\pi} \int_{0}^{2} \frac{V_{P}}{R_{L}} \sin(t) dt = -\frac{V_{P}}{\pi R_{L}} [\cos(t)]_{0}^{2} = \frac{V_{P}}{\pi R_{L}}$$
(4)

Where

$$V_{\rm P} = \sqrt{2 \, {\rm P_L} \, {\rm R_L}} \tag{5}$$

Therefore,

$$P_{SUP} = \frac{V_{CC} V_P}{\pi R_L} + V_{CC} I_{CC(q)}$$
(6)

$$\begin{split} &\mathsf{P}_{L} = \mathsf{Power \ delivered \ to \ load \ (per \ channel)} \\ &\mathsf{P}_{SUP} = \mathsf{Power \ drawn \ from \ power \ supply} \\ &\mathsf{V}_{LRMS} = \mathsf{RMS \ voltage \ on \ the \ load} \\ &\mathsf{R}_{L} = \mathsf{Load \ resistance} \\ &\mathsf{V}_{P} = \mathsf{Peak \ voltage \ on \ the \ load} \\ &\mathsf{I}_{CC} \mathsf{avg} = \mathsf{Average \ current \ drawn \ from \ the \ power \ supply} \\ &\mathsf{I}_{CC}(\mathsf{q}) = \mathsf{Quiescent \ current \ (per \ channel)} \\ &\mathsf{V}_{CC} = \mathsf{Power \ supply \ voltage \ (total \ supply \ voltage \ = \ 30 \ V \ if \ running \ on \ a \ \pm 15 \text{-V \ power \ supply} \\ &\mathsf{\eta} = \mathsf{Efficiency \ of \ a \ SE \ amplifier} \end{split}$$

For stereo operation, the efficiency does not change because both  $P_L$  and  $P_{SUP}$  are doubled, affecting the amount of power dissipated by the package in the form of heat.

A simple formula for calculating the power dissipated,  $P_{DISS}$ , is shown in Equation 7:

 $P_{DISS} = (1 - \eta) P_{SUP}$ 

 $T_A Max = T_J Max - \theta_{JA} P_{DISS}$ 

(7)

In stereo operation,  $\mathsf{P}_{\mathsf{SUP}}$  is twice the quantity that is present in mono operation.

The maximum ambient temperature,  $T_A$ , depends on the heat-sinking ability of the system.  $R_{\theta JA}$  for a 20-pin DWP, whose thermal pad is properly soldered down, is shown in *Thermal Information*. Also see Figure 18.

(8)



#### TPA6120A2

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015



www.ti.com

#### 10.2.1.3 Application Performance Plots


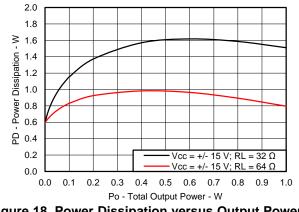


Figure 18. Power Dissipation versus Output Power

#### 10.2.2 High Fidelity Smartphone Application

A new trend in portable applications are termed "Hifi Smartphones". In these systems, a standard portable audio codec continues to be used for telephony, while a separate, higher performance DAC and Headphone Amplifier is used for music playback.

Figure 19 shows a complete circuit schematic for such a system. The digital audio is fed into a high performance DAC. The PCM5242, a Burr-Brown product from TI, is a 32-bit, stereo DAC.

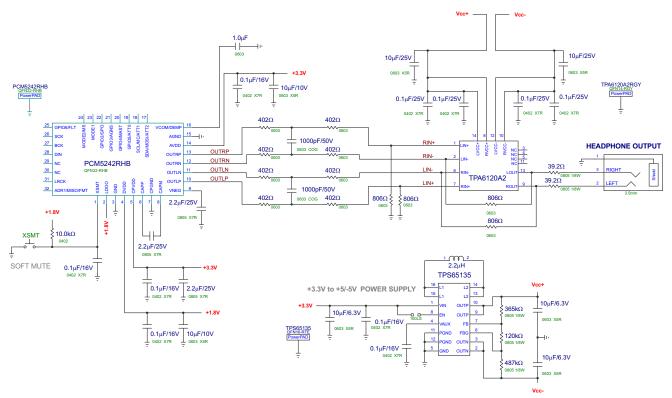





**Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com

www.ti.com

TPA6120A2 SLOS431B – MARCH 2004 – REVISED FEBRUARY 2015

#### 10.2.2.1 Design Requirements

INSTRUMENTS

- ±5V Operation from an over system power supply of 3.3V
- Stereo differential inputs (DAC is differential)
- Be transparent to the user. (DAC SNR and THD+N performance all the way to the headphone)

#### 10.2.2.2 Detailed Design Procedure

For optimal performance, the TPA6120A2 is configured for use with differential inputs, stereo use, and a gain of 1V/V.

The TPA6120A2 requires a bipolar power supply to drive a ground centered output. The application employs a TPS65135 DC-DC converter that generates ±5V from a single 3.3V supply.

The PCM5242 DAC is configured for a 1VRMS output so that clipping is avoided should the 3.3V power supply sag. The PCM5242 offers a ground centered output, so that no DC blocking capacitors are required between it and the TPA6120A2.

Resistor values around the TPA6120A2 of  $806\Omega$  and a  $39.2\Omega$  were found to offer the optimal conditions of SNR and THD. Starting with 1K $\Omega$  resistors for input and feedback, and 10 $\Omega$  output resistance, the feedback resistance was lowered to increase the amount of current in the feedback network. The output resistance was increased to ease the load on the headphone amplifier when low impedance headphones are connected. Both of these additions contribute to the excellent SNR and THD of the TPA6120A2 in such a low voltage application.

Note that the 0.1-uF X7R capacitors are placed at every supply pin of the TPA6120A2.

Using such a solution makes the TPA6120A2 transparent in the circuit, even into a low impedance 320hm load.

The remaining steps are the same as those described in *Resistor Values*.

#### 10.2.2.3 Application Performance Plots

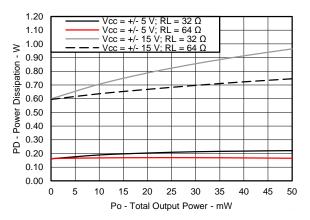


Figure 20. Power Dissipation versus Power Output - 50mW Scale

In this particular application, the TPA6120A2's performance is transparent and the performance of the system is dictated by the PCM5242 DAC.



#### TPA6120A2

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015



www.ti.com

### **11** Power Supply Recommendations

#### **11.1 Independent Power Supplies**

The TPA6120A2 consists of two independent high-fidelity amplifiers. Each amplifier has its own voltage supply, allowing the user to leave one of the amplifiers off, saving power, reducing the generated heat, and reducing crosstalk.

Although the power supplies are independent, there are some limitations. When both amplifiers are used, the same voltage must be applied to each amplifier. For example, if the left channel amplifier is connected to a  $\pm 12$ -V supply, the right channel amplifier must also be connected to a  $\pm 12$ -V supply. If the device is connected to a different supply voltage, it may not operate properly and consistently.

When the use of only one amplifier is preferred, it must be the left amplifier. The voltage supply to the left amplifier is also responsible for internal start-up and bias circuitry of the device. Regardless of whether one or both amplifiers are used, the  $V_{CC-}$  pins of both amplifiers must always be at the same potential.

To power down the right channel amplifier, disconnect the  $V_{CC+}$  pin from the power source.

The two independent power supplies can be tied together on the board to receive their power from the same source.

#### 11.2 Power Supply Decoupling

As with any design, proper power supply decoupling is essential. Decoupling prevents noise from entering the device via the power traces and provides the extra power the device can sometimes require in a rapid fashion, preventing the device from being momentarily current-starved. Both of these functions serve to reduce distortion, leaving a clean, uninterrupted signal at the output.

Bulk decoupling capacitors should be used where the main power is brought to the board. Smaller capacitors should be placed as close as possible to the actual power pins of the device. Because the TPA6120A2 has four power pins, use four surface mount capacitors. Both types of capacitors should be low ESR.



www.ti.com

#### TPA6120A2 SLOS431B – MARCH 2004 – REVISED FEBRUARY 2015

## 12 Layout

#### 12.1 Layout Guidelines

Proper board layout is crucial to getting the maximum performance out of the TPA6120A2.

A ground plane should be used on the board to provide a low inductive ground connection. Having a ground plane underneath traces adds capacitance, so care must be taken when laying out the ground plane on the underside of the board (assuming a 2-layer board). The ground plane is necessary on the bottom for thermal reasons.

Stray capacitance can still make its way onto the sensitive outputs and inputs. Place components as close as possible to the pins and reduce trace lengths. See Figure 21 and Figure 22. Place the feedback resistor and the series output resistor extremely close to the pins. The input resistor should also be placed close to the pin. If the amplifier is to be driven in a noninverting configuration, ground the input close to the device so the current has a short, straight path to the PowerPAD (gnd).

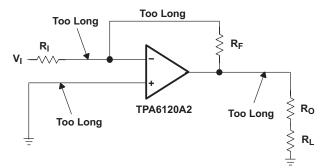


Figure 21. Layout That Can Cause Oscillation

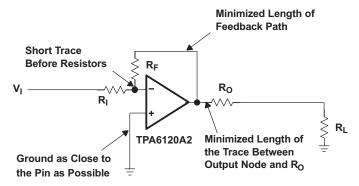


Figure 22. Layout Designed To Reduce Capacitance On Critical Nodes



#### TPA6120A2

SLOS431B – MARCH 2004 – REVISED FEBRUARY 2015



www.ti.com

### 12.2 Layout Example

This is part of a 4-layer board, where ground, V+, V- are on the bottom and two middle traces, respectively. Key items to note in this layout:

- 1. R4 and R3 are the output resistors in the schematic. They are sized as 0603 surface mount resistors instead of 0402 for their thermal capacity, as they will be dissipating heat, depending on the output power.
- 2. Traces are kept as short as possible to avoid any capacitance or oscillation issues.
- 3. In systems that may be using the DWP package with through hole resistors, it's strongly suggested that the input and output pins and components do not have a ground plane directly beneath them, to avoid stray capacitance.

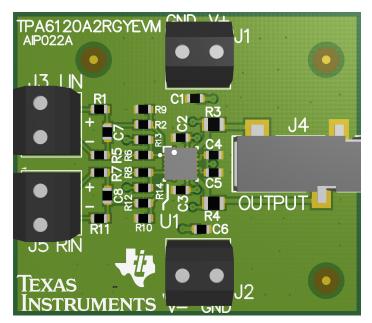


Figure 23. PCB Layout Example

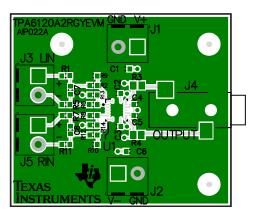


Figure 24. Example PCB Layout, Top Layer and Silkscreen, Top View

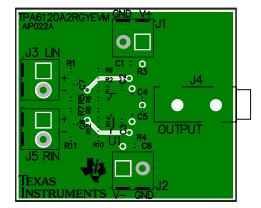


Figure 25. Example PCB Layout, Middle-1 Layer and Silkscreen, Top View



**Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com

www.ti.com

TPA6120A2 SLOS431B – MARCH 2004 – REVISED FEBRUARY 2015

#### Layout Example (continued)

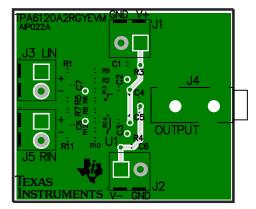


Figure 26. Example PCB Layout, Middle-2 Layer and Silkscreen, Top View

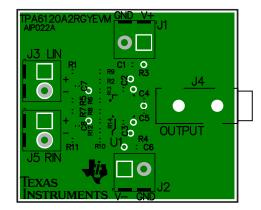


Figure 27. Example PCB Layout, Bottom Layer and Silkscreen, Top View



#### TPA6120A2

SLOS431B - MARCH 2004 - REVISED FEBRUARY 2015



www.ti.com

#### **13 Device and Documentation Support**

#### **13.1 Documentation Support**

#### 13.1.1 Related Documentation

Headphone Amplifier Parametric Table

SoundPlus<sup>™</sup> High Performance Audio Operational Amplifiers, SBOS058

#### 13.2 Trademarks

All trademarks are the property of their respective owners.

#### 13.3 Electrostatic Discharge Caution



These devices have limited built-in ESD protection. The leads should be shorted together or the device placed in conductive foam during storage or handling to prevent electrostatic damage to the MOS gates.

#### 13.4 Glossary

SLYZ022 — TI Glossary.

This glossary lists and explains terms, acronyms, and definitions.

#### 14 Mechanical, Packaging, and Orderable Information

The following pages include mechanical packaging and orderable information. This information is the most current data available for the designated devices. This data is subject to change without notice and revision of this document. For browser-based versions of this data sheet, refer to the left-hand navigation.




**DWP0020B** 

**Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com

# PACKAGE OUTLINE

PowerPAD<sup>™</sup> SOIC - 2.65 mm max height

PLASTIC SMALL OUTLINE

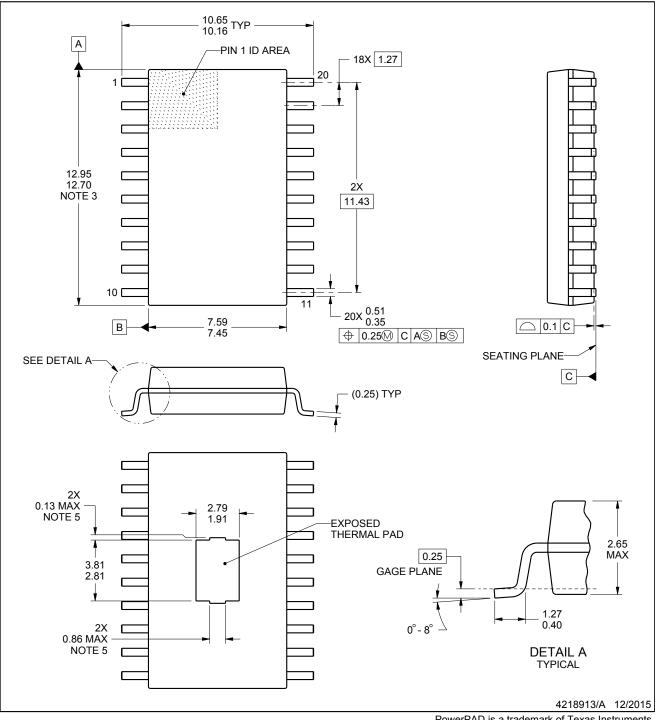

NOTES:

PowerPAD is a trademark of Texas Instruments.

- 1. All linear dimensions are in millimeters. Any dimensions in parenthesis are for reference only. Dimensioning and tolerancing per ASME Y14.5M.
- 2. This drawing is subject to change without notice.

3. This dimension does not include mold flash, protrusions, or gate burrs. Mold flash, protrusions, or gate burrs shall not

exceed 0.15 mm per side.

4. Features may not present.






**DWP0020B** 

# **EXAMPLE BOARD LAYOUT**

# PowerPAD<sup>™</sup> SOIC - 2.65 mm max height

PLASTIC SMALL OUTLINE

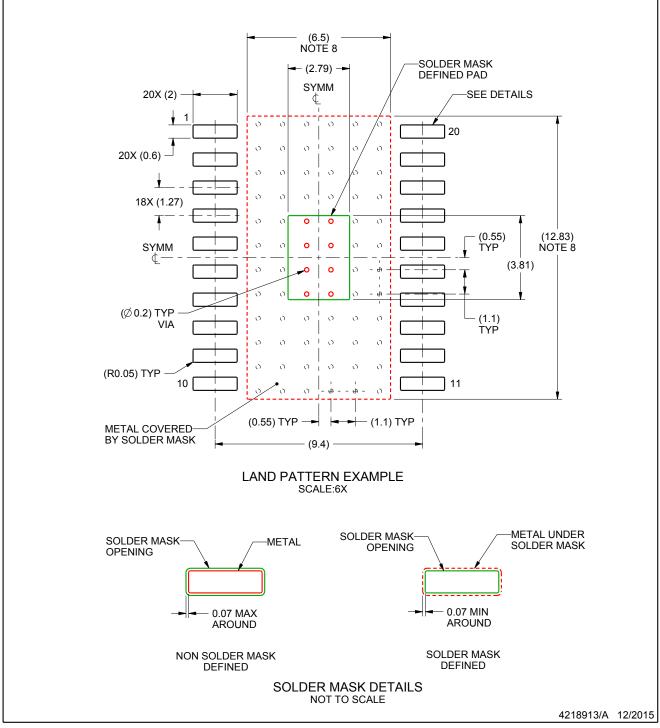

NOTES: (continued)

5. Publication IPC-7351 may have alternate designs.

6. Solder mask tolerances between and around signal pads can vary based on board fabrication site.

7. This package is designed to be soldered to a thermal pad on the board. For more information, see Texas Instruments literature

- numbers SLMA002 (www.ti.com/lit/slma002) and SLMA004 (www.ti.com/lit/slma004).
- 8. Size of metal pad may vary due to creepage requirement.






# **EXAMPLE STENCIL DESIGN**

# **DWP0020B**

# PowerPAD<sup>™</sup> SOIC - 2.65 mm max height

PLASTIC SMALL OUTLINE

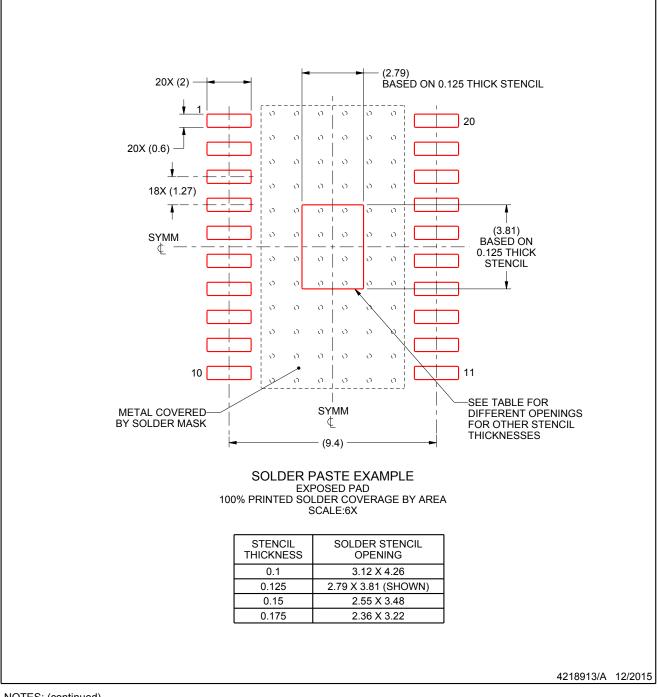

NOTES: (continued)


9. Laser cutting apertures with trapezoidal walls and rounded corners may offer better paste release. IPC-7525 may have alternate design recommendations.

10. Board assembly site may have different recommendations for stencil design.





# **MECHANICAL DATA**

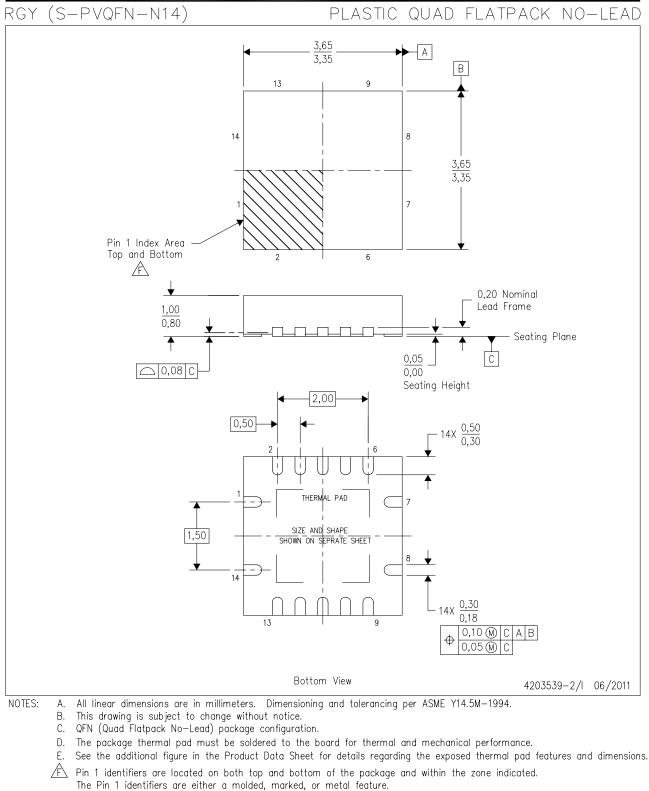


G. Package complies to JEDEC MO-241 variation BA.





# THERMAL PAD MECHANICAL DATA

 
# RGY (S-PVQFN-N14) PLASTIC QUAD FLATPACK NO-LEAD THERMAL INFORMATION This package incorporates an exposed thermal pad that is designed to be attached directly to an external heatsink. The thermal pad must be soldered directly to the printed circuit board (PCB). After soldering, the PCB can be used as a heatsink. In addition, through the use of thermal vias, the thermal pad can be attached directly to the appropriate copper plane shown in the electrical schematic for the device, or alternatively, can be attached to a special heatsink structure designed into the PCB. This design optimizes the heat transfer from the integrated circuit (IC). For information on the Quad Flatpack No-Lead (QFN) package and its advantages, refer to Application Report, QFN/SON PCB Attachment, Texas Instruments Literature No. SLUA271. This document is available at www.ti.com. The exposed thermal pad dimensions for this package are shown in the following illustration. 6 Exposed Thermal Pad 1 7 2,05±0,10 14 8 13 g -2,05±0,10 Bottom View Exposed Thermal Pad Dimensions 4206353-2/P 03/14







# LAND PATTERN DATA

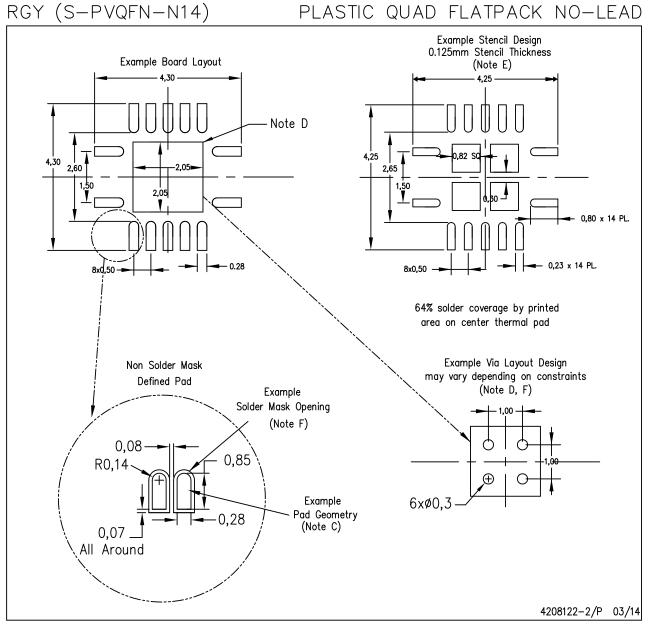

NOTES:

- S: A. All linear dimensions are in millimeters.
  - B. This drawing is subject to change without notice.
  - C. Publication IPC-7351 is recommended for alternate designs.
  - D. This package is designed to be soldered to a thermal pad on the board. Refer to Application Note, Quad Flat-Pack QFN/SON PCB Attachment, Texas Instruments Literature No. SLUA271, and also the Product Data Sheets for specific thermal information, via requirements, and recommended board layout. These documents are available at www.ti.com <htp://www.ti.com>.
  - E. Laser cutting apertures with trapezoidal walls and also rounding corners will offer better paste release. Customers should contact their board assembly site for stencil design recommendations. Refer to IPC 7525 for stencil design considerations.
  - F. Customers should contact their board fabrication site for minimum solder mask web tolerances between signal pads.





10-Sep-2014

#### PACKAGING INFORMATION

www.ti.com

Orderable Device	Status	Package Type	Package	Pins	Package	Eco Plan	Lead/Ball Finish	MSL Peak Temp	Op Temp (°C)	Device Marking	Samples
	(1)		Drawing		Qty	(2)	(6)	(3)		(4/5)	
TPA6120A2DWP	ACTIVE	SO PowerPAD	DWP	20	25	Green (RoHS & no Sb/Br)	CU NIPDAU	Level-2-260C-1 YEAR	-40 to 85	6120A2	Samples
TPA6120A2DWPG4	ACTIVE	SO PowerPAD	DWP	20	25	Green (RoHS & no Sb/Br)	CU NIPDAU	Level-2-260C-1 YEAR	-40 to 85	6120A2	Samples
TPA6120A2DWPR	ACTIVE	SO PowerPAD	DWP	20	2000	Green (RoHS & no Sb/Br)	CU NIPDAU	Level-2-260C-1 YEAR	-40 to 85	6120A2	Samples
TPA6120A2DWPRG4	ACTIVE	SO PowerPAD	DWP	20	2000	Green (RoHS & no Sb/Br)	CU NIPDAU	Level-2-260C-1 YEAR	-40 to 85	6120A2	Samples
TPA6120A2RGYR	ACTIVE	VQFN	RGY	14	3000	Green (RoHS & no Sb/Br)	CU NIPDAU	Level-2-260C-1 YEAR	-40 to 85	6120A2	Samples
TPA6120A2RGYT	ACTIVE	VQFN	RGY	14	250	Green (RoHS & no Sb/Br)	CU NIPDAU	Level-2-260C-1 YEAR	-40 to 85	6120A2	Samples

<sup>(1)</sup> The marketing status values are defined as follows:

ACTIVE: Product device recommended for new designs. LIFEBUY: TI has announced that the device will be discontinued, and a lifetime-buy period is in effect. NRND: Not recommended for new designs. Device is in production to support existing customers, but TI does not recommend using this part in a new design.

PREVIEW: Device has been announced but is not in production. Samples may or may not be available. OBSOLETE: TI has discontinued the production of the device.

(2) Eco Plan - The planned eco-friendly classification: Pb-Free (RoHS), Pb-Free (RoHS Exempt), or Green (RoHS & no Sb/Br) - please check http://www.ti.com/productcontent for the latest availability information and additional product content details.

TBD: The Pb-Free/(Green conversion plan has not been defined. Pb-Free (RoHS): TI's terms "Lead-Free" or "Pb-Free" mean semiconductor products that are compatible with the current RoHS requirements for all 6 substances, including the requirement that lead not exceed 0.1% by weight in homogeneous materials. Where designed to be soldered at high temperatures, TI Pb-Free products are suitable for use in specified lead-free processes. Pb-Free (RoHS Exempt): This component has a RoHS exemption for either 1) lead-based flip-chip solder bumps used between the die and package, or 2) lead-based die adhesive used between the die and leadframe. The component is otherwise considered Pb-Free (RoHS compatible) as defined above. Green (RoHS & no Sh/Br): Ti defines "Green" to mean Pb-Free (RoHS compatible), and free of Bromine (Br) and Antimony (Sb) based flame retardants (Br or Sb do not exceed 0.1% by weight in homogeneous material)

(3) MSL, Peak Temp. - The Moisture Sensitivity Level rating according to the JEDEC industry standard classifications, and peak solder temperature.

(4) There may be additional marking, which relates to the logo, the lot trace code information, or the environmental category on the device.

(5) Multiple Device Markings will be inside parentheses. Only one Device Marking contained in parentheses and separated by a "~" will appear on a device. If a line is indented then it is a continuation of the previous line and the two combined represent the entire Device Marking for that device

Addendum-Page 1



10-Sep-2014

(6) Lead/Ball Finish - Orderable Devices may have multiple material finish options. Finish options are separated by a vertical ruled line. Lead/Ball Finish values may wrap to two lines if the finish value exceeds the maximum column width.

Important Information and Disclaimer: The information provided on this page represents TI's knowledge and belief as of the date that it is provided. TI bases its knowledge and belief on information provided by third parties, and makes no representation or warranty as to the accuracy of such information. Efforts are underway to better integrate information from third parties. TI has taken and continues to take reasonable steps to provide representative and accurate information but may not have conducted destructive testing or chemical analysis on incoming materials and chemicals. TI and TI suppliers consider certain information to be proprietary, and thus CAS numbers and other limited information may not be available for release.

In no event shall TI's liability arising out of such information exceed the total purchase price of the TI part(s) at issue in this document sold by TI to Customer on an annual basis.

Addendum-Page 2




www.ti.com




# PACKAGE MATERIALS INFORMATION

11-Nov-2014

## TAPE AND REEL INFORMATION

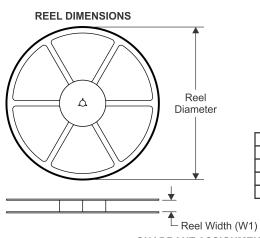


\*All dimensions are nominal

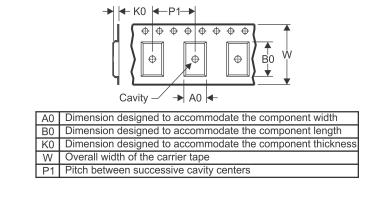

TAPE DIMENSIONS
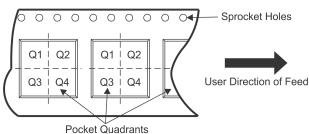
### QUADRANT ASSIGNMENTS FOR PIN 1 ORIENTATION IN TAPE



Device		Package Drawing		SPQ	Reel Diameter (mm)	Reel Width W1 (mm)	A0 (mm)	B0 (mm)	K0 (mm)	P1 (mm)	W (mm)	Pin1 Quadrant
TPA6120A2DWPR	SO Power PAD	DWP	20	2000	330.0	24.4	10.8	13.3	2.7	12.0	24.0	Q1
TPA6120A2RGYR	VQFN	RGY	14	3000	330.0	12.4	3.75	3.75	1.15	8.0	12.0	Q2
TPA6120A2RGYT	VQFN	RGY	14	250	180.0	12.4	3.75	3.75	1.15	8.0	12.0	Q2




www.ti.com

**Distributor of Texas Instruments: Excellent Integrated System Limited** Datasheet of TPA6120A2DWP - IC AMP AUDIO .08W HIFI 20SOPWR Contact us: sales@integrated-circuit.com Website: www.integrated-circuit.com



# PACKAGE MATERIALS INFORMATION

11-Nov-2014

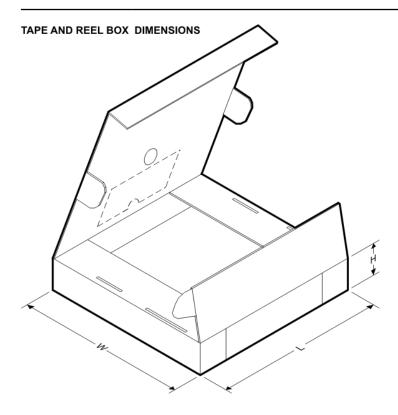

\*All dimensions are nominal

Device	Package Type	Package Drawing	Pins	SPQ	Length (mm)	Width (mm)	Height (mm)
TPA6120A2DWPR	SO PowerPAD	DWP	20	2000	367.0	367.0	45.0
TPA6120A2RGYR	VQFN	RGY	14	3000	367.0	367.0	35.0
TPA6120A2RGYT	VQFN	RGY	14	250	210.0	185.0	35.0



#### **IMPORTANT NOTICE**

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products		Applications	
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial
Interface	interface.ti.com	Medical	www.ti.com/medical
Logic	logic.ti.com	Security	www.ti.com/security
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com		
OMAP Applications Processors	www.ti.com/omap	TI E2E Community	e2e.ti.com
Wireless Connectivity	www.ti.com/wirelessconne	ctivity	

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2016, Texas Instruments Incorporated